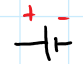
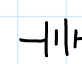

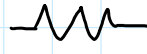



A Basic Circuit

- A source of energy: Battery, Cell,  , 
- path for electrons: wire 
- A device that uses the energy: resistor  : light 

dry: 1.5V battery
wet: car battery

- Battery - source of energy (makes the electrons move)
- units volts
 - Potential Difference
 - Electromotive Force, \mathcal{E} mf, \mathcal{E}

- Resistors - uses the energy $\begin{cases} \text{heat} \\ \text{light} \end{cases}$
- measured in ohms, Ω , 25Ω


Current: the number of electrons flowing past a point in a given time.

: $Q = ne$ (# of electrons $\times 1.6 \times 10^{-19} \text{C}$)

: $I = \frac{Q}{t}$ units $\frac{\text{C}}{\text{s}}$, 1 Ampere = 1Amp = 1A

: Conventional current flows from the positive terminal of the battery, through the circuit, to the negative terminal.

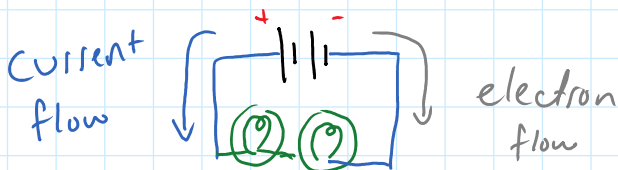: Electrons flow from negative to positive






flow



Ohm's Law

$$V = IR$$

$$I = \frac{V}{R}$$

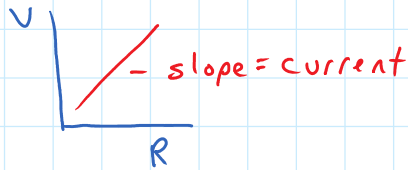

Power : the rate at which electrical work is done

: watts (w)

$$P = VI$$

$$= (IR)I$$

power output from a source

ex ($V = 3.0\text{v}$, $I = 200\text{mA} = .2\text{A}$)

$$P = (3.0)(.2) = .6\text{w}$$

$$P = I^2 R$$

← power used by a device (light, resistor)

Energy = $E = P \cdot t$

units $\begin{cases} \rightarrow = (\text{w} \cdot \text{s}) = \text{J} \\ \rightarrow = (\text{kw} \cdot \text{H}) = \text{kw} \cdot \text{H} \end{cases}$

ex: A 12v car battery transfers 48C of charge in 8.0s.

a) $I = \frac{Q}{t} = \frac{48\text{C}}{8\text{s}} = 6.0\text{A}$

b) $R = \frac{V}{I} = \frac{12\text{v}}{6.0\text{A}} = 2\Omega$

c) Power out put of the battery $P = V \cdot I = (12\text{v})(6\text{A}) = 72\text{w}$

ex: A 1400w microwave is used for 45min per day in a cafe.

Energy used $\begin{cases} \rightarrow P \cdot t = (1400\text{w})(2700\text{s}) = 3.78 \times 10^6 \text{J} \\ \rightarrow P \cdot t = (1.4\text{kw})(.75\text{Hr}) = 1.05 \text{kw} \cdot \text{H} \end{cases}$

$\sim 10^6 / \text{kw} \cdot \text{H}$

Hw. p. 180 #1-3, 184 #1-4