

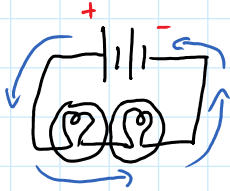


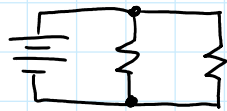
Series Circuit: - one device is followed by another  
 - one path for the electrons/current to travel



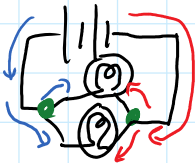
Parallel Circuit - split, junction in circuit  
 - more than one path for current/electrons



Combo

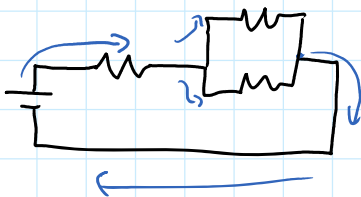


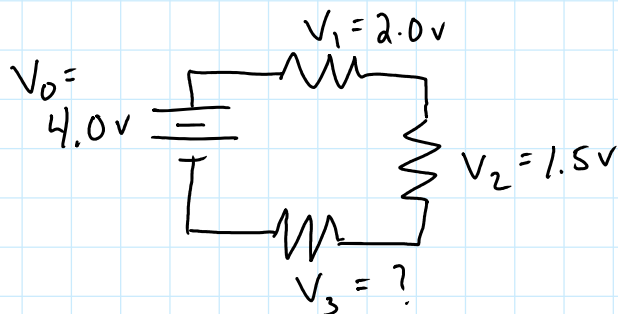The Voltage Law: The sum of the voltage increases (battery)  
 = the sum of the voltage decrease/drop (light/  
 resistor) for one complete path




$$V_0 = V_1 + V_2 + V_3$$


$$4.0V = 2.0V + 1.5V + 0.5V$$

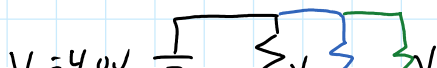

$$V_0 = V_1 + V_2 + V_3 = 4.0V$$

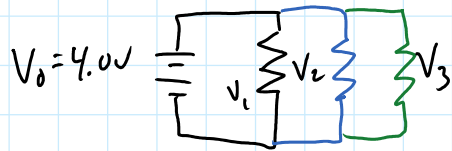


$$V_0 = V_1 + V_2 + V_3 = 4.0V$$

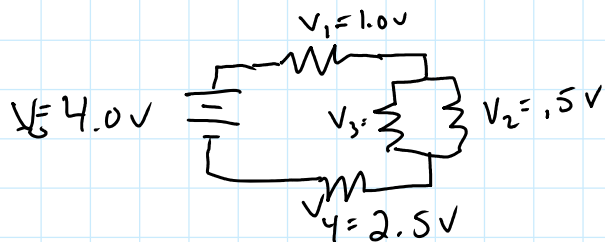

$$V_3 = 0.5V$$
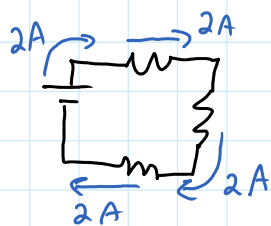
## Current Law

Series: no junction or split, the  $I$  out of the source (battery) =  $I$  through the entire circuit.




Parallel: Total  $I$  into a junction = the sum of the  $I$  in each parallel portion



## Resistance in a Circuit


Series

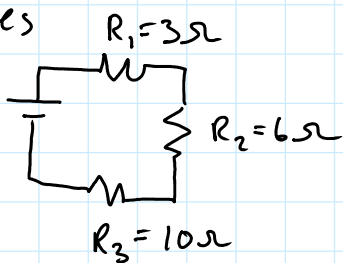

$$\begin{aligned} R_{eq} &= R_1 + R_2 + R_3 \\ &= 3\Omega + 6\Omega + 10\Omega \\ R_{eq} &= 19\Omega \end{aligned}$$

$$I = \frac{V}{R}$$

Parallel

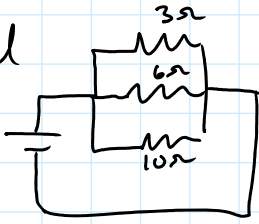

$$I_0 = I_1 + I_2 + I_3$$

$$\frac{V_0}{R} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\frac{1}{R_{eq}} = \frac{1}{3\Omega} + \frac{1}{6\Omega} + \frac{1}{10\Omega}$$

$$= \frac{10}{30} + \frac{5}{30} + \frac{3}{30}$$

$$\frac{1}{R_{eq}} = \frac{18}{30}, R_{eq} = \frac{30}{18} = 1.67\Omega$$

ex

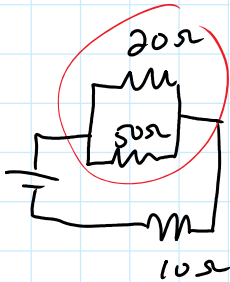

Find  $R_{eq}$  for the circuit.

$$\frac{1}{20} + \frac{1}{50}$$

$$\frac{5}{100} + \frac{2}{100} = \frac{7}{100} = \frac{1}{R} \quad R = \frac{100}{7} = 14.3\Omega$$



$$10 + 14.3\Omega$$

$$R_{eq} = 24.3\Omega$$

P1 & 3 of booklet.

P.1 a)  $10\Omega$

b)  $0.8\Omega$

c)  $4\Omega$

d)  $7\Omega$

e)  $.69\Omega$

f)  $2.7\Omega$

P.3 1) B

2)  $4.0\text{ C}$

3) I-X, C-M

4)  $V_1 = 5\text{ V}, V_2 = 1\text{ V}$

5) A

6) C