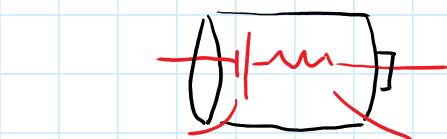


Internal Resistance & Terminal Voltage


Tuesday, May 22, 2018 12:37 PM

In a battery, the material that produces Emf (Voltage) has some resistance. This reduces the output voltage of the battery when current flows thru it



Emf, \mathcal{E}
produced by
the chemicals

internal
resistance
(r)

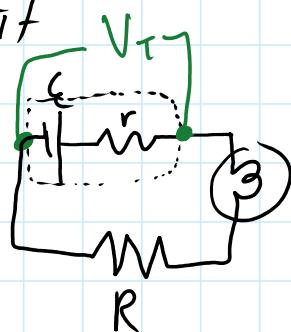

Terminal
Voltage

$$V_T = \mathcal{E} - Ir$$

Used when charging the battery

Used when powering
a device

ex

$$\mathcal{E} = 6.0\text{V}$$

$$r = 0.5\Omega$$

$$I = 1\text{A}$$


Find V_T

$$\begin{aligned} V_T &= \mathcal{E} - Ir \\ &= 6.0\text{V} - (1\text{A})(0.5\Omega) \\ &= 5.5\text{V} \end{aligned}$$

ex : A cell phone battery is charged using 200mA and has $r = 0.8\Omega$. Find \mathcal{E} if $V_T = 6.0\text{V}$. 0.20A

$$\begin{aligned} V_T &= \mathcal{E} + Ir \\ 6.0\text{V} &= \mathcal{E} + (0.20\text{A})(0.8\Omega) \\ &\dots \end{aligned}$$

Ex

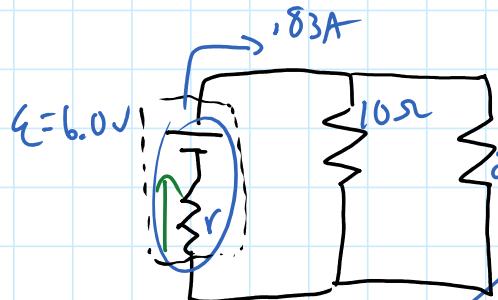

$$E = 5.84 \text{ V}$$

Treat as just another resistor
Find $r = ?$, V_T

$$V_o = 6.0 \text{ V} \quad I_o = 0.83 \text{ A}$$

$$R_{eq} = 7.2 \Omega$$

$$R_1 = 10 \Omega \quad \left\{ \frac{1}{10} + \frac{1}{50} \right\}$$

$$R_2 = 20 \Omega \quad \left\{ \frac{2}{20} + \frac{1}{20} = \frac{3}{20} \right\}$$

$$r = 0.5 \Omega$$

$$V_1 = 5.58 \quad I_1$$

$$V_2 = 5.58 \quad I_2$$

$$V_3 = 4 \Omega \quad I_3 = 0.83 \text{ A}$$

$$\begin{aligned} V_T &= E - Ir \\ &= 6.0 \text{ V} - (0.83 \text{ A})(0.5 \Omega) \\ &= 5.58 \text{ V} \end{aligned}$$