
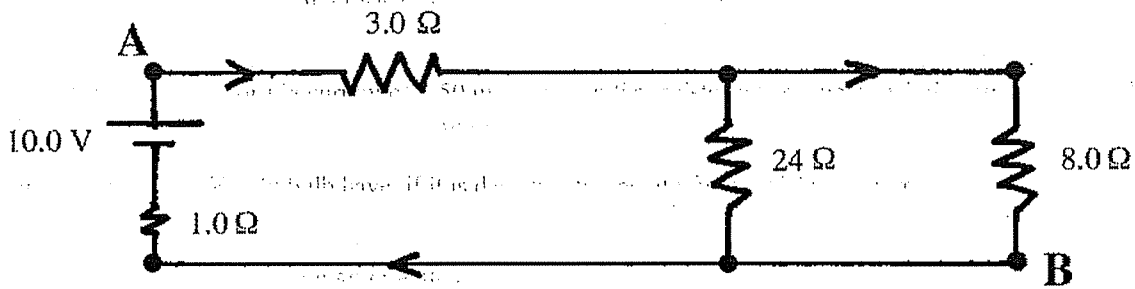


Electric Circuits

- What is the current in a circuit if 12 C of charge pass a point in 1.5 s?
8.0 A $I = \frac{Q}{t} = \frac{12C}{1.5s}$
- What is the voltage between the ends of a resistor if 360 J of energy is expended as heat for every 6.0 C of charge that pass through the resistor?
 $E = P \cdot t = V \cdot I \cdot t = V \cdot \frac{Q}{t} \cdot t = V \cdot Q$ $V = \frac{E}{Q} = \frac{360}{6} = 60V$
- What is the resistance of a resistor if a current of 1.50 mA exists in the resistor when a potential difference of 45.0 V is applied to the ends of the resistor?
 $V = IR, R = \frac{V}{I}$ $30k\Omega = \frac{45}{.0015} = 30k\Omega$
- What resistance must a 60.0 W light bulb have, if it is designed to operate from a 120.0 V source?
 $P = V \cdot I = V \left(\frac{V}{R}\right) = \frac{V^2}{R}$ $R = \frac{V^2}{P} = \frac{120^2}{60} = 240\Omega$
- A battery with an internal resistance of 0.50 Ω delivers 1.50 A to a light bulb of resistance 3.0 Ω . What is the EMF of the battery?
 $R_T = 3.5\Omega$
 $I = 1.5A$
 $V = IR$
- Three resistors are connected in series with a 24.0 V battery. If the resistors are 2.0 Ω , 4.0 Ω and 6.0 Ω , what is the potential difference across the 4.0 Ω resistor?
 $R_T = 12\Omega$ $8.0V$ $I_T = 2A$ $V_4 = (2)(4) = 8V$
- Three resistors are in parallel, and a current of 36.0 A enters the parallel network. If the resistors have resistances of 2.0 Ω , 3.0 Ω and 6.0 Ω , what current exists in the 3.0 Ω resistor?
 $R_T = 1\Omega$ $V_T = 36V$ $I = \frac{V}{R} = \frac{36}{3} = 12A$

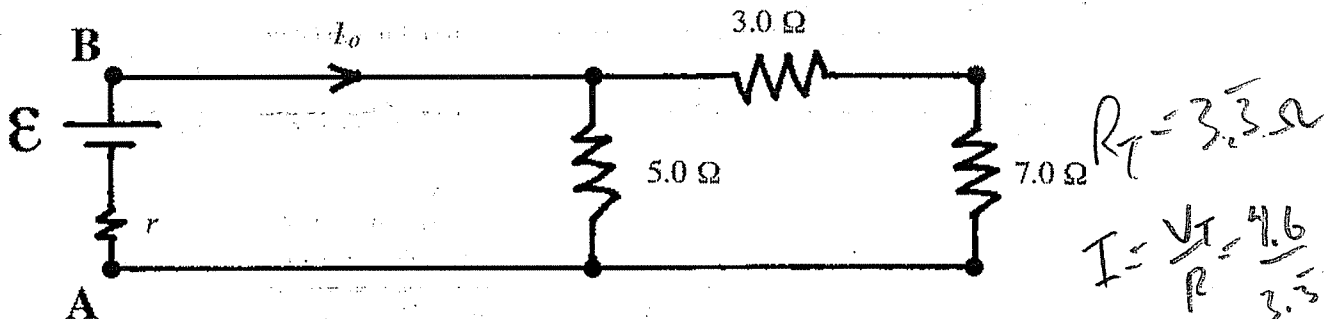


- What is the equivalent resistance of the above circuit?
 $\frac{1}{24} + \frac{1}{8} \rightarrow 6\Omega + 4\Omega = 10.0\Omega$
- What current exists at A?
 $\frac{V}{R} = \frac{10}{10} = 1$ 1.0 A
- What is the potential difference between the ends of the 8.0 Ω resistor?
6.0 V $V_2 = 3V$ $V_1 = 1V$ so $V = 6V$
- What current exists at B?
 $I = \frac{V}{R} = \frac{6}{8} = .75A$ 0.75 A




- The EMF of the battery above is 6.00 V, and the terminal voltage V_{AB} is 4.60 V.

$R_T = 3.3\Omega$
 $I = \frac{V_T}{R} = \frac{4.6}{3.3} = 1.38A$

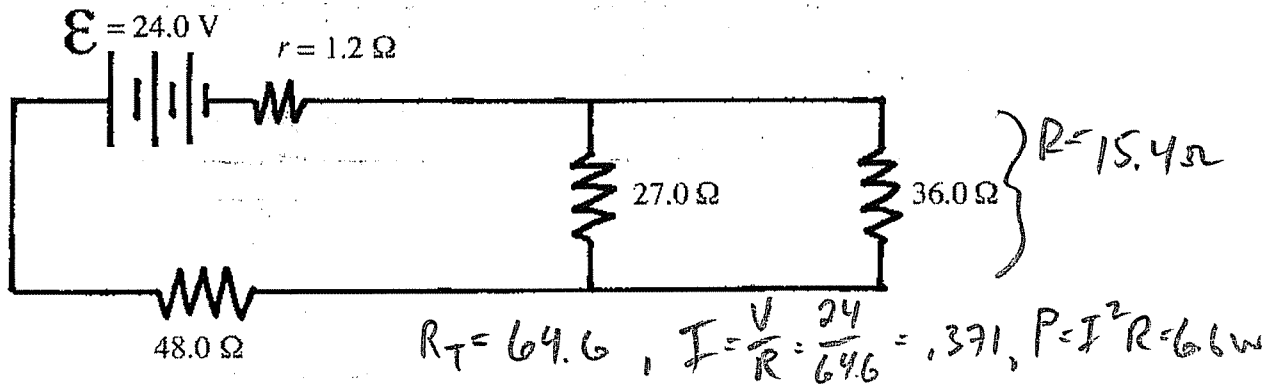
- (a) What is the total current I_0 ? 1.38 A
 (b) What is the internal resistance r ? $V = \mathcal{E} - Ir$, $6.0 - 4.6 = (1.38)r$ 1.01 Ω



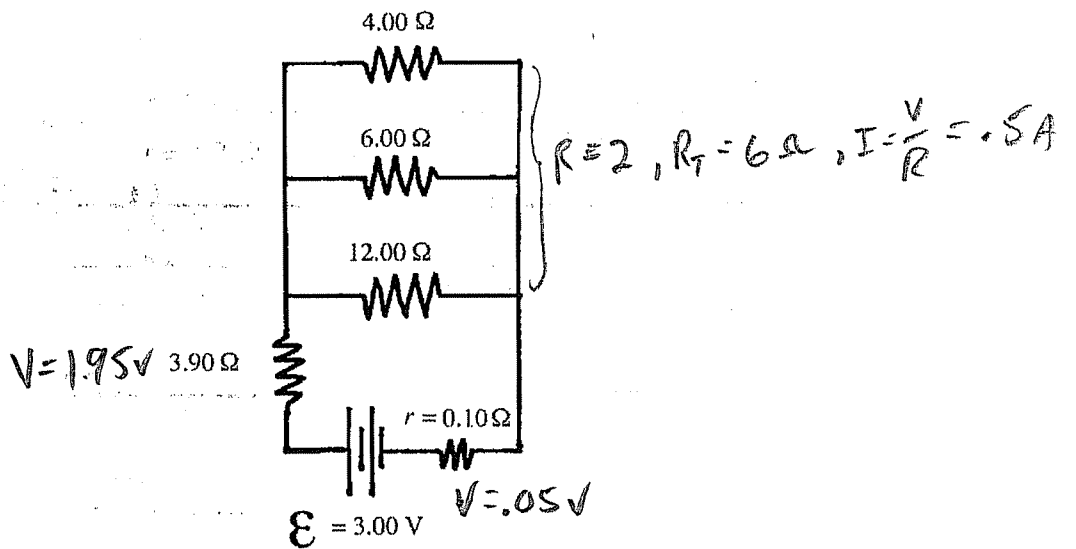10. If the EMF of the battery above is 24.0 V and its internal resistance r is 1.2 Ω , what power is dissipated in the 48.0 Ω resistor? 6.6 W



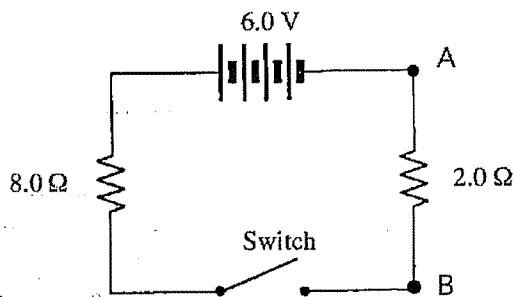11. (a) What is the voltage across the 6.0 Ω resistor? 1.0 V
 (b) What current exists in the 12 Ω resistor? 0.083 A $I = \frac{V}{R} = \frac{1}{12}$
12. A dry cell has an EMF of 1.500 V. When it is connected in series with a 1.20 Ω resistor, the current through it is 0.750 A. What is the internal resistance of the dry cell? 0.800 Ω
 $R_T = \frac{V}{I} = \frac{1.5}{0.75} = 2 \Omega - 1.2 \Omega = 0.8 \Omega$
13. Three 60-W light bulbs are connected in parallel with a 120 V source. What total current must the source supply to the three light bulbs? 1.5 A
 $P = 180 W = IV$ $I = \frac{180 W}{120 V} = 1.5 A$
- 14.




The switch in the above diagram is open. What is the potential difference V_{AB} across the 2.0 Ω resistor?

0V



0 V

Assignment

Multiple Choice

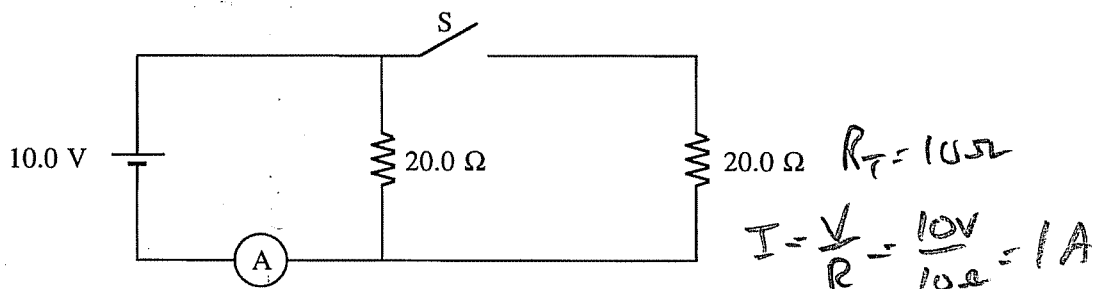


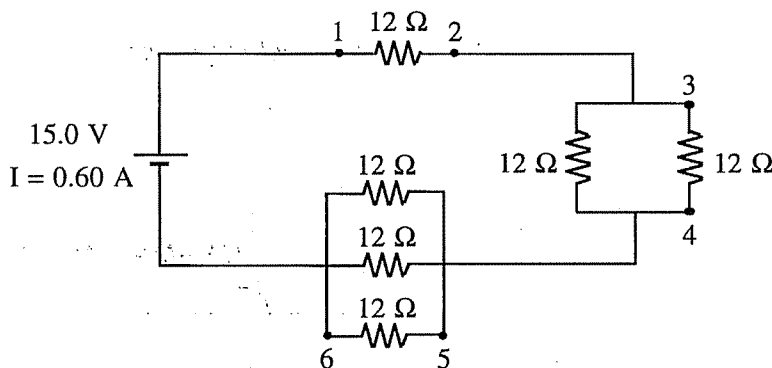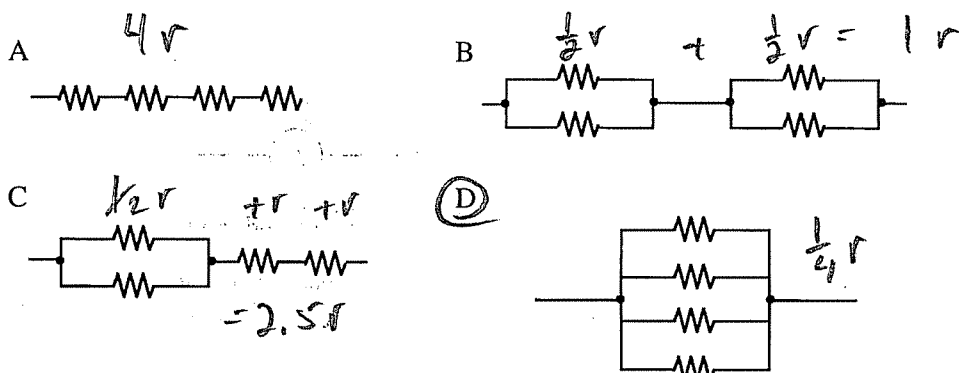- The current through A is 0.50 A when the switch S is open. What will the current through A be when the switch S is closed?
 - 0 A
 - 0.25 A
 - 0.50 A
 - 1.0 A
- Which one of the following arrangements of four identical resistors will have the least resistance?





- Where is the most power dissipated in this circuit?
 - Between 1 and 2.
 - Between 3 and 4.
 - Between 5 and 6.
 - Power dissipated is the same in all three situations.

$P = I^2 R$
I is greatest between 1 & 2

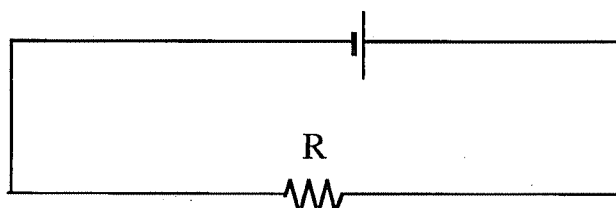

4. In this circuit, if you wish to measure the current through resistor R and the voltage between the ends of resistor R , where should the ammeter and voltmeter be placed?

	ammeter	voltmeter
A	in series ✓	in series
B	in series ✓	in parallel ✓
C	in parallel	in parallel ✓
D	in parallel	in series

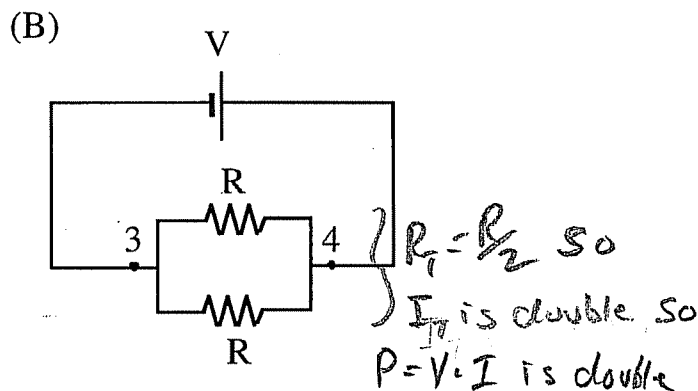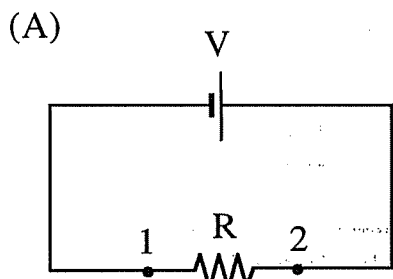

5. The power dissipated in circuit (A) in resistor R between 1 and 2 is P . In circuit (B) the same source voltage is used, but an identical resistor R is added in parallel with the first resistor. How much power will be dissipated between 3 and 4?

A. $\frac{1}{4}P$


B. $\frac{1}{2}P$

C. P

D. $2P$

E. $4P$

Open-Ended Questions

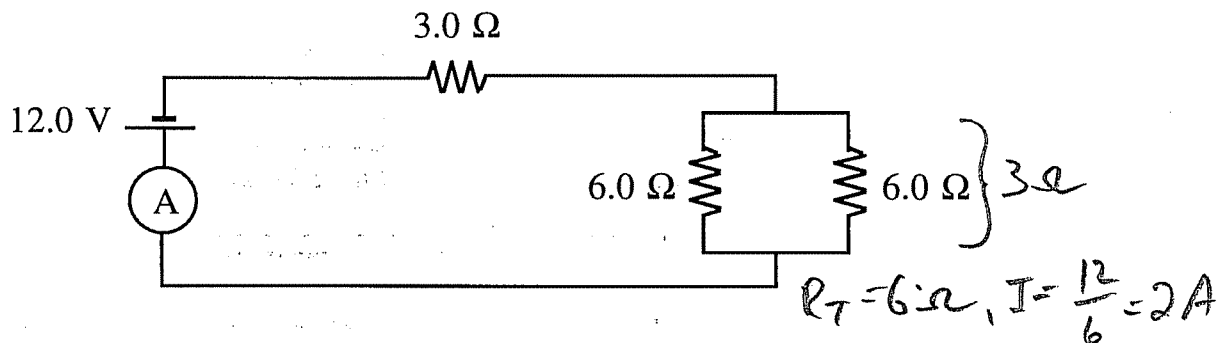

6. What is the current in the ammeter A?


7. A 1500 W kettle is connected to a 110 V source. What is the resistance of the kettle element?

$$P = V \cdot I = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$$

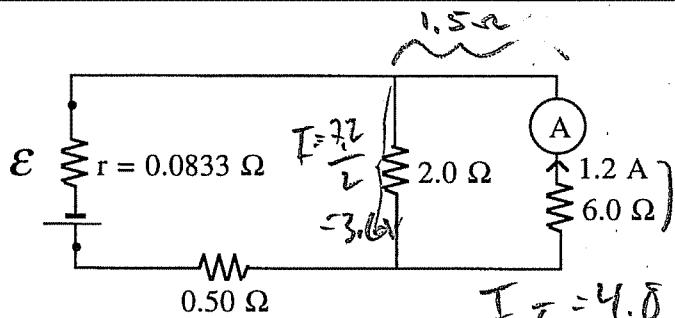8. A flashlight contains a battery of two cells in series, with a bulb of resistance 12.0Ω . The internal resistance of each cell is 0.260Ω . If the potential difference across the bulb is 2.88 V , what is the EMF of each cell?


Handwritten solution for question 8:

$$R_T = 12.52 \Omega, I = \frac{V}{R} = \frac{2.88}{12} = .24 \text{ A} \quad V_T = (.24)(12.52) = 3.00 \text{ V} \div 2 = 1.5 \text{ V}$$



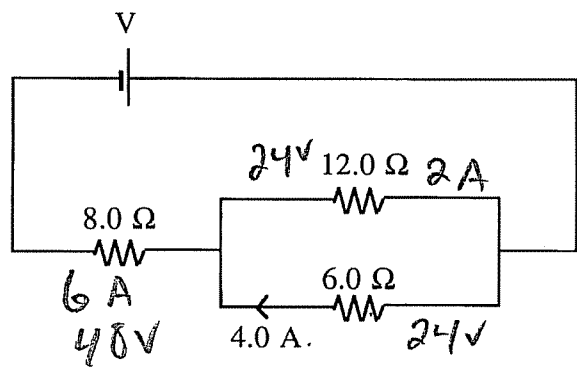9. What is the EMF of the battery if the current in A is 1.2 A, and the internal resistance of the battery is 0.0833 Ω?


$I_T = 4.0 \text{ A}, R_T = 2.0833 \Omega, V_T = IR = 10 \text{ V}$



10. What is the voltage V of the power supply?


$48 + 24 = 72 \text{ V}$

$\mathcal{E} = 12.00 \text{ V}$

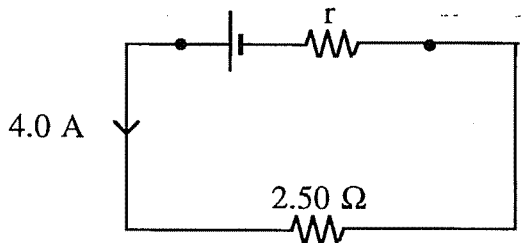

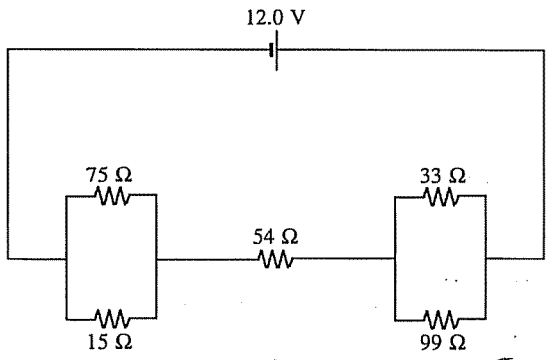11. What is the internal resistance of the battery?

$R_T = \frac{V_T}{I_T} = \frac{12}{4} = 3 \Omega, r = .5 \Omega$



12. (a) What is the equivalent resistance of this circuit?


(b) What is the current through the 54 Ω resistor?

(c) How much power is dissipated in the 54 Ω resistor?


$I = \frac{V}{R} = \frac{12}{91} = .13 \text{ A}$

$12.5 \Omega + 54 \Omega + 24.75 = 91.25 \Omega$

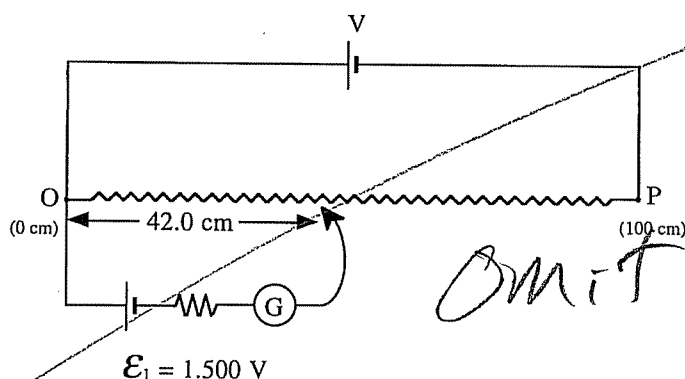$P = I^2 R = (.13)^2 54 \Omega = .93 \text{ W}$



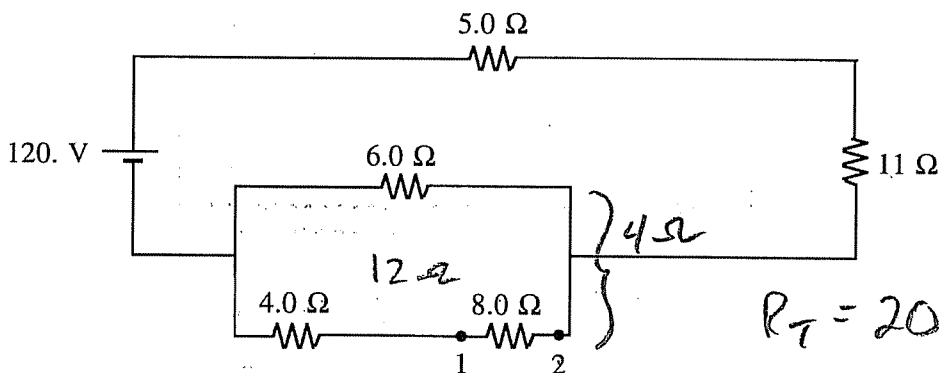13. A potentiometer with a standard cell of EMF $\mathcal{E}_1 = 1.500 \text{ V}$ is 'balanced' when the contact is 42.0 cm from O. When \mathcal{E}_1 is replaced with a second cell with EMF \mathcal{E}_2 , balance is achieved at 48.0 cm from O. What is the magnitude of EMF \mathcal{E}_2 ?



14. (a) What is the voltage across the 8.0 Ω resistor (between 1 and 2)?
 (b) How much power is dissipated in the 5.0 Ω resistor?

1. D 2. D 3. A 4. B 5. D
 6. 2.0 A
 7. 8.1 Ω
 8. 1.50 V
 9. 10.0 V
 10. 72 V
 11. 0.50 Ω
 12. (a) 91
 (b) 0.13 A
 (c) 0.93 W
 13. 1.71 V
 14. (a) 16 V
 (b) $1.8 \times 10^2 \text{ W}$

$$R_T = 20 \Omega, I_T = \frac{120}{20} = 6 \text{ A}$$

$$V_{11} = IR = (6)(4) = 24 \text{ V}$$

$$I_{1:2} = \frac{V}{R} = \frac{24 \text{ V}}{12} = 2 \text{ A}$$

$$V_{1:2} = IR = (2 \text{ A})(8) = 16 \text{ V}$$

$$P = I^2 R = 6^2 \cdot 5 = 180 \text{ W}$$