

Current Electricity

Monday, May 15, 2017 10:35 AM

When electrons flow in a wire, they produce an electric current.

The current is a measure of the amount of charge passing a point in a given time

$$I = \frac{Q}{t}$$

t - sec
Q - Coulombs

$I = \frac{C}{S}$, 1 Ampere
1 Amp
1 A

ex Calculate the current through a toaster if it takes $\frac{900\text{c}}{\text{Q}}$ to toast your bread in 2.0 min

$$I = \frac{Q}{t} = \frac{900\text{c}}{120\text{s}} = 7.5\text{A}$$

ex How many electrons flow through a wire in 1.0 sec if 2 A of current is flowing?

$$Q = ne$$

$$t = 1.0 \text{ sec}$$

$$I = 2.0 \text{ A}$$

$$I = \frac{Q}{t}$$



$$2.0 = \frac{Q}{1.0\text{s}}$$

$$Q = 2.0 \text{ C} = ne$$

$$2.0 \text{ C} = n(1.6 \times 10^{-19} \text{ C})$$

$$n = 1.25 \times 10^{19} \text{ electrons}$$

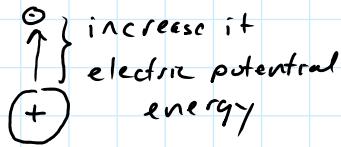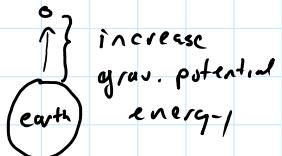Voltage - Potential Difference (Change in Potential)



} similar to the voltage output of a battery

Voltage is measured in volts



Electric Circuit


A Basic Circuit

- A source of energy: Battery, Cell

schematic

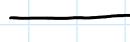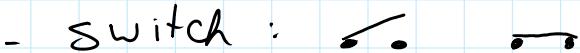

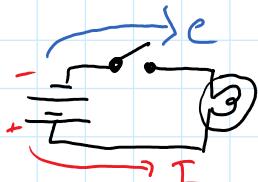- dry wet
- A device that uses the energy: light 
 - : resistor 
 - A closed path: wire 
 - switch: 



Battery: Source of energy (makes the electrons flow)

: output is measured in Volts


: Potential Difference

: Electromotive Force, ϵ_{mf} , ϵ

Current : $I = \frac{Q}{t}$, Amps

: Current flows from the positive terminal through the circuit to the negative terminal

: Electrons flow away from negative to the positive.

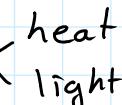Resistors : use the energy  / heat / light

: measured in Ohm's, Ω

12Ω , 150Ω

Ohm's law

$$V = IR$$

$$I = \frac{V}{R}$$



- slope = $I = \text{current}$

Determine the resistance of a toaster that uses 120V and 7.5A.

$$V = 120 \text{ V}$$

$$I = 7.5 \text{ A}$$

$$V = IR$$

$$\frac{120}{7.5} = \frac{(7.5)(R)}{7.5}$$

$$R = 16 \Omega$$

A 60Ω stove requires 240V to operate. Determine the current through the stove.

P. 454 #5-7, 8a,