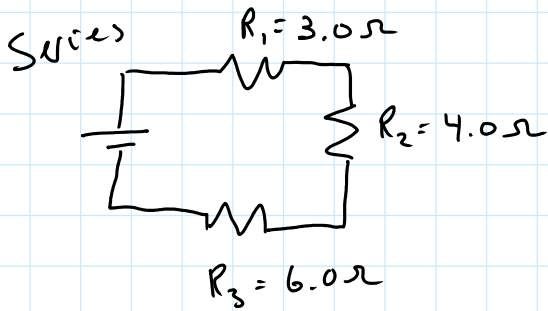


Resistance in a Series and Parallel Circuit

Wednesday, May 17, 2017 10:37 AM




The 3 resistors can be replaced with one equivalent resistor

$$R_{eq} = R_1 + R_2 + R_3 + \dots \text{ for series}$$

$$= 3\Omega + 4\Omega + 6\Omega$$

$$= 13\Omega$$

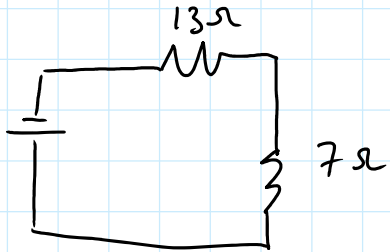

$$R_{eq} = 20\Omega$$

a) 10Ω

Parallel



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$= \frac{1}{3} + \frac{1}{4} + \frac{1}{6}$$

$$= \frac{4}{12} + \frac{3}{12} + \frac{2}{12}$$

$$\frac{1}{R_{eq}} = \frac{9}{12}$$

$$R_{eq} = \frac{12}{9} = 1.\bar{3}\Omega$$

X^{-1}

$\frac{1}{X}$

$$.333 + .25 + .167 = .75$$

$$\frac{1}{R_{eq}} = .75$$

$$.75^{-1} = 1.33$$


b) $\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{4}$ $\frac{1}{R_{eq}} = 1.25$, $R_{eq} = 0.8\Omega$


c) $\frac{1}{R_{eq}} = \frac{1}{8} + \frac{1}{8}$ $R_{eq} = 4\Omega$

e) 0.69Ω


f) 2.73Ω

d) combo

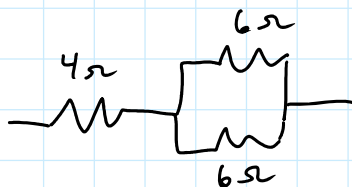

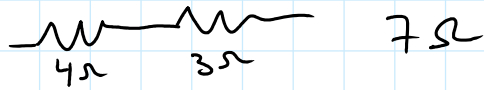


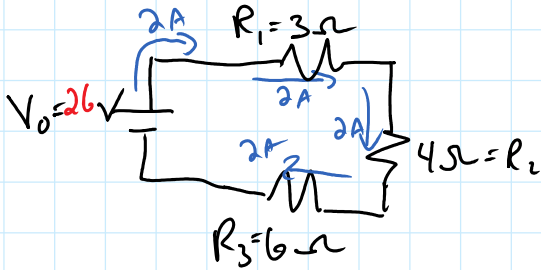Determine the V, I, R in the following circuit $I = \frac{V}{R}$



$V_0 = 26V$	$I_0 = 2A$	$R_{eq} = 13\Omega$
$V_1 = 6V$	$I_1 = 2A$	$R_1 = 3\Omega$
$V_2 = 8V$	$I_2 = 2A$	$R_2 = 4\Omega$
$V_3 = 12V$	$I_3 = 2A$	$R_3 = 6\Omega$

H.W.

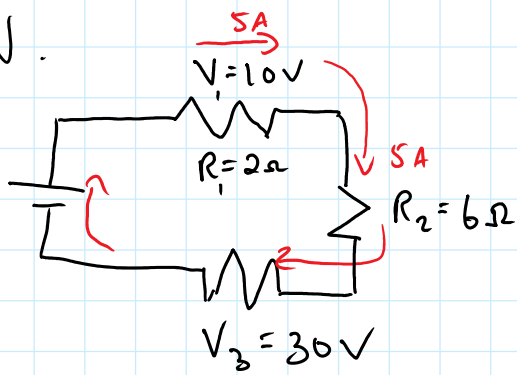

$V_0 = 70V$	$I_0 = 5A$	$R_{eq} = 14\Omega$
$V_1 = 10V$	$I_1 = 5A$	$R_1 = 2\Omega$
$V_2 = 30V$	$I_2 = 5A$	$R_2 = 6\Omega$
$V_3 = 30V$	$I_3 = 5A$	$R_3 = 6\Omega$

$$R_{eq} = R_1 + R_2 + R_3$$

$$\left. \begin{aligned} V = IR, \quad I = \frac{V}{R}, \quad R = \frac{V}{I} \end{aligned} \right\}$$