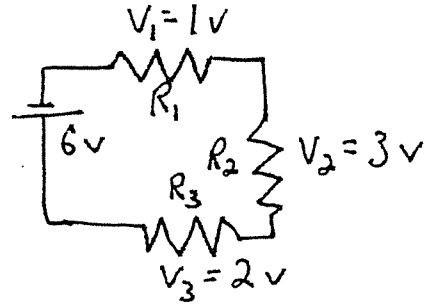


Voltage, Resistance and Current in a Series Circuit


VOLTAGE

From Kirchoffs Law, the total voltage increase is equal to the total voltage decrease. Consider the following circuit.

The voltage increase from the battery is 6 v.
The decreases from each of the resistors adds up to 6 v.



What is V_1 in the following circuit?

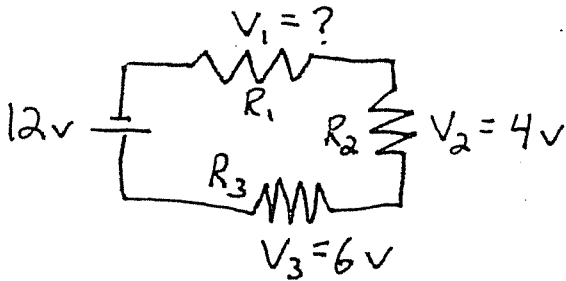

$V_1 =$


The voltage decrease or voltage drop across each resistor depends on the value of the resistors in the circuit. It is necessary to find the TOTAL RESISTANCE of a circuit.

RESISTANCE


To find the total resistance of a series circuit, sometimes written R_T , you need to add up all the resistors. So

$$R_T = R_1 + R_2 + R_3 + \dots$$

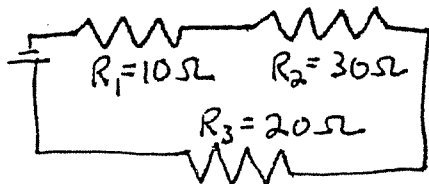
In this circuit the total resistance is $10 \Omega + 30 \Omega + 20 \Omega = 60 \Omega$




Find R_T for the following circuits

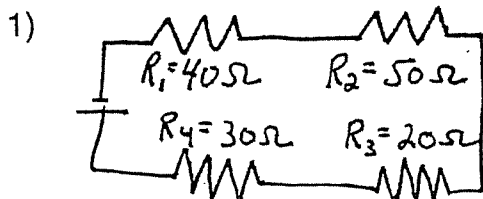

$R_T =$

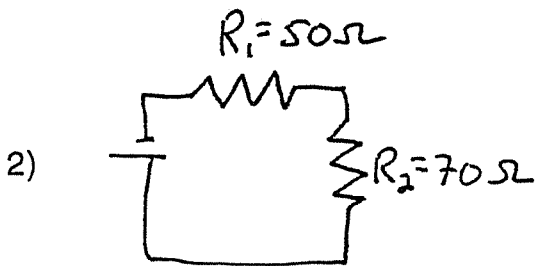

$R_T =$

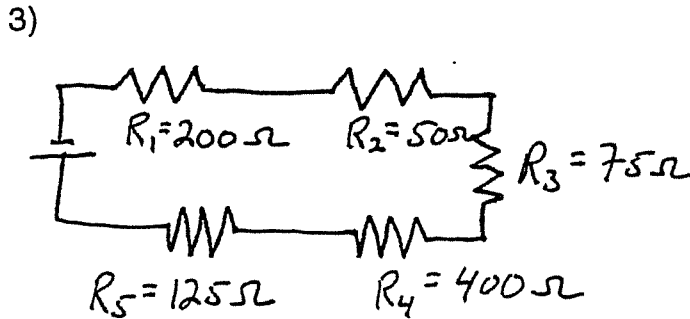


$R_T =$

CURRENT


The current in a series circuit is the same throughout the whole circuit, because there are no junctions.

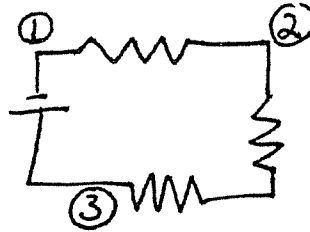If the current at point 1 is 2 Amps, then the current at point 2 is 2 Amps and at point 3 is 2 Amps.




If the current at point 1 is 50 mA, then

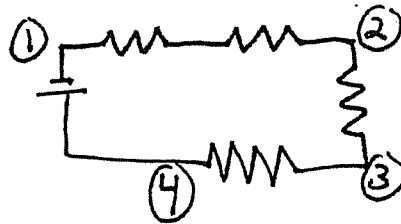- what is the current at point 2? _____
- what is the current at point 3? _____
- what is the current at point 4? _____



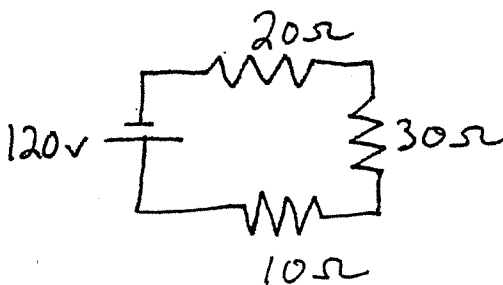To find the current in a series circuit, use Ohms Law. Remember $V = I \times R$ and $I = V \div R$. Consider the following.




$$V_T = 120 \text{ v (from the battery)}$$


$$R_T = 20 \Omega + 30 \Omega + 10 \Omega = 60 \Omega$$

$$\text{So } I_T = \frac{V_T}{R_T} = \frac{120 \text{ v}}{60 \Omega} = 2 \text{ A}$$


Find I for each of the following:

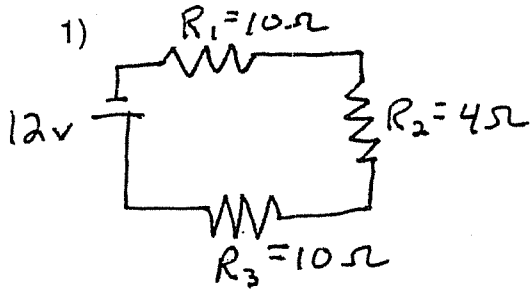

$V_T =$
 $R_T =$
 $I_T =$

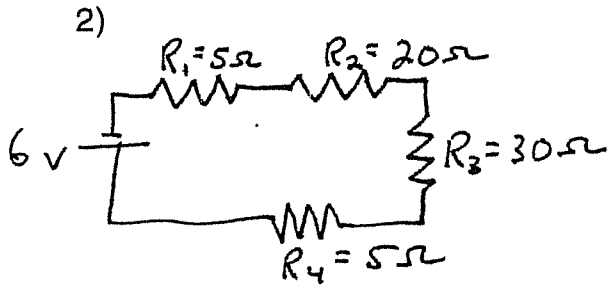


$V_T =$
 $R_T =$
 $I_T =$

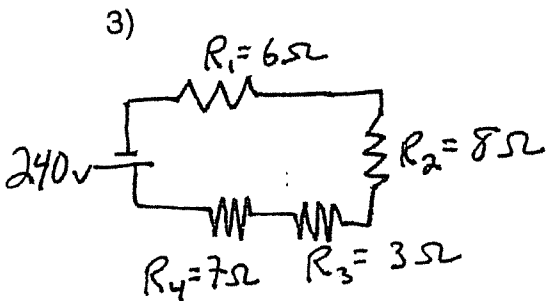

$V_T =$
 $R_T =$
 $I_T =$

The current which flows in the circuit also flows in each resistor. This is how the **voltage decrease** for each resistor is calculated.

Consider the previous example:

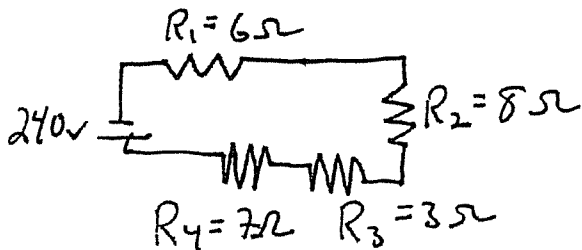

$V_T = 240 \text{ v}$, $R_T = 24 \Omega$, $I_T = 10 \text{ Amps}$.

The voltage decrease across R_1 is determined by Ohms Law, $V_1 = I \times R_1$.

The current through R_1 is 10 amps and the resistance is 6Ω so $V_1 = 10 \text{ a} \times 6 \Omega = 60 \text{ v}$.

Similarly the voltage decrease across R_2 will be


$$V_2 = 10 \text{ amps} \times 8 \Omega = 80 \text{ v},$$

for R_3 $V_3 = 10 \text{ amps} \times 3 \Omega = 30 \text{ v},$

for R_4 $V_4 = 10 \text{ amps} \times 7 \Omega = 70 \text{ v}.$

If these voltage decreases are added up, the total is $60\text{ v} + 80\text{ v} + 30\text{ v} + 70\text{ v} = 240\text{ v}$, which is the same as the voltage increase or the voltage of the battery. This is a way to check to make sure you did it right.

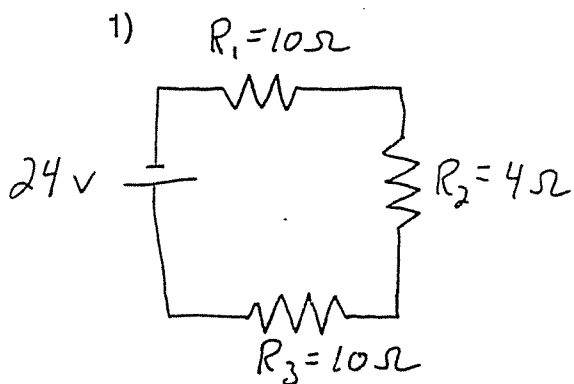Find the voltage decreases for the following circuits.



$V_T =$ $R_T =$ $I_T =$


Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$

Total of all Voltage decreases ___

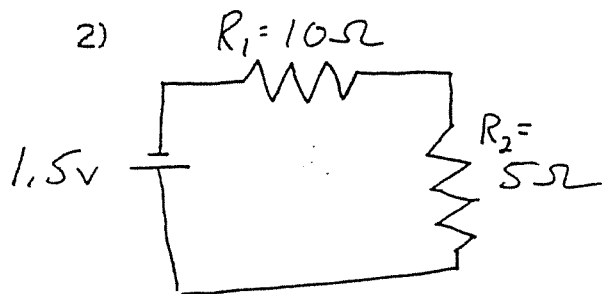


$V_T =$ $R_T =$ $I_T =$

Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Total of all Voltage decreases ___

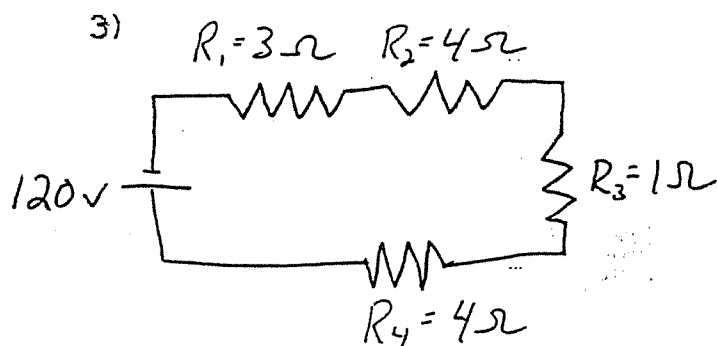

$V_T =$ $R_T =$ $I_T =$

Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$


Voltage decrease for R_4 , $V_4 =$

Total of all Voltage decreases ___


Voltage, Current and Resistance in a Parallel Circuit

VOLTAGE

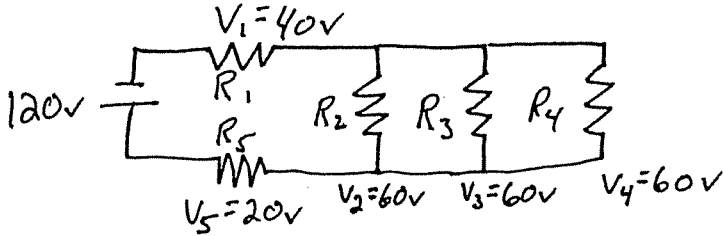From Kirchoffs Law, the voltage increase in a circuit is equal to the voltage decreases for a complete path.




Find

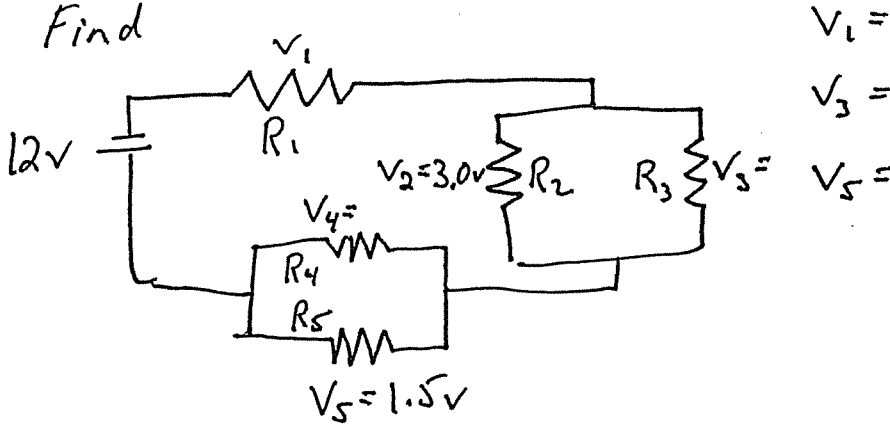


CURRENT

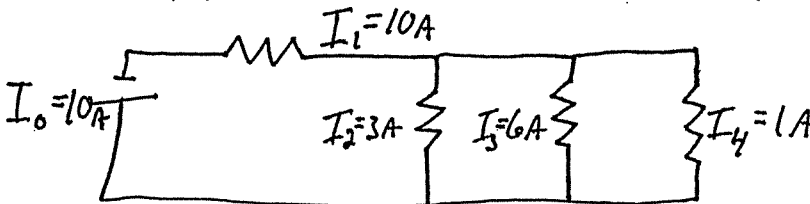Again Kirchoffs Laws are used. The current entering a junction must equal the current in the junction and exiting it.



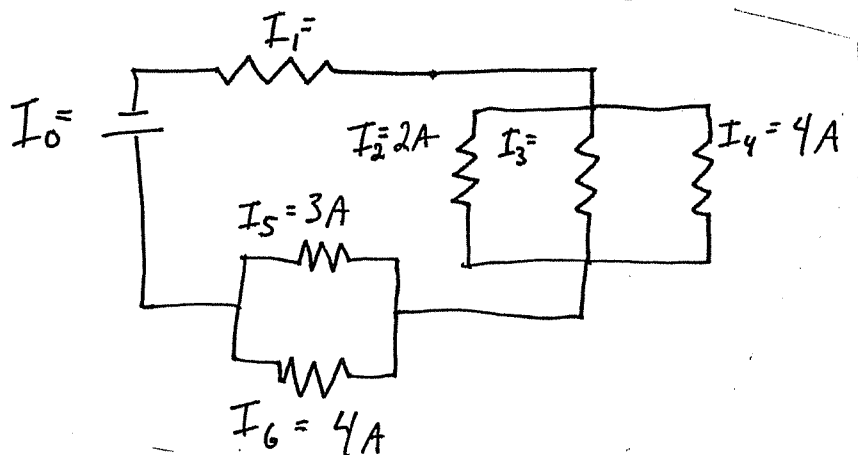Find the current in the following parts of the circuit.




$I_0 =$
 $I_1 =$
 $I_2 =$

RESISTANCE

To find the total resistance, R_T , in a parallel circuit use the following equation.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

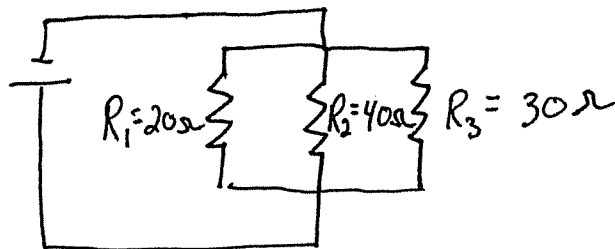This is a tough equation to use. Please follow the outline shown below.



1) Write out the equation above, substituting in the values for R_1 , R_2 , R_3 , etc. So:

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{40} + \frac{1}{30}$$

2) Convert the fractions to decimals. So: $\frac{1}{R_T} = \frac{1}{20} + \frac{1}{40} + \frac{1}{30}$ becomes

$$\frac{1}{R_T} = 0.05 + 0.025 + 0.0\bar{3}$$

3) Add up the decimal numbers, so: $0.05 + 0.025 + 0.033 = 0.108$

$$\frac{1}{R_T} = 0.108$$

This is **NOT** the final answer!!

4) Take the reciprocal of both sides.

$$\frac{R_T}{1} = \frac{1}{0.108}$$

5) Divide the fraction ($1 \div 0.108 = 9.26$)


This **IS** the answer. $R_T = 9.26 \Omega$

There are other ways of doing this, but this method is the simplest.

Questions:

1) Find the total resistance in the following parallel circuits.

a)

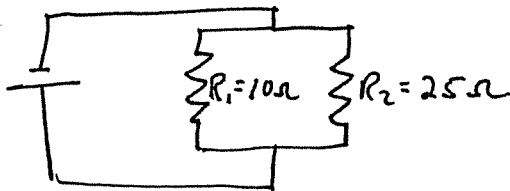


Step 1) $\frac{1}{R_T} = \frac{1}{10} + \frac{1}{25}$

5) $R_T = \quad \Omega$


2) $\frac{1}{R_T} = 0.1 + 0.04$

3) $\frac{1}{R_T} = 0.14$

4) $\frac{R_T}{1} = \frac{1}{0.14}$

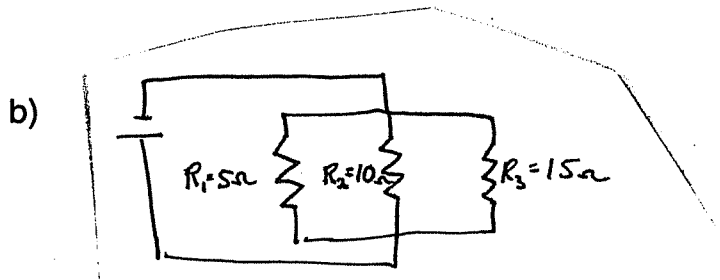

$R_T =$

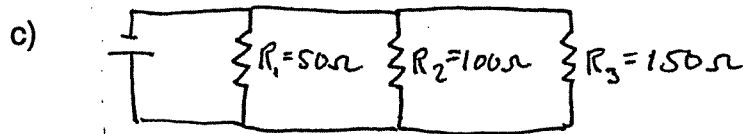

$R_T =$

d) a circuit with a $20\ \Omega$, $40\ \Omega$, $60\ \Omega$ and $80\ \Omega$ resistors all in parallel.

$R_T =$

e) a circuit with a $25\ \Omega$, $50\ \Omega$, $75\ \Omega$, $100\ \Omega$ and $200\ \Omega$ resistors all in parallel.

$R_T =$

f) Calculate the total resistance of

i) 2, $50\ \Omega$ resistors in parallel.

$R_T =$

ii) 3, $50\ \Omega$ resistors in parallel.

$R_T =$

iii) 4, $50\ \Omega$ resistors in parallel.

$R_T =$

Series Circuit Worksheet

Name: _____

1) Unit Conversion: Amps to milliAmps etc.

Remember $1000 \text{ mA} = 1 \text{ A}$

$1000 \text{ mV} = 1 \text{ V}$

$1 \text{ mA} = 0.001 \text{ A}$

$1 \text{ mV} = 0.001 \text{ V}$

a) $2 \text{ A} = \underline{\hspace{2cm}} \text{ mA}$

b) $0.2 \text{ A} = \underline{\hspace{2cm}} \text{ mA}$

c) $15 \text{ A} = \underline{\hspace{2cm}} \text{ mA}$

d) $0.007 \text{ A} = \underline{\hspace{2cm}} \text{ mA}$

e) $6000 \text{ mA} = \underline{\hspace{2cm}} \text{ A}$

f) $750 \text{ mA} = \underline{\hspace{2cm}} \text{ A}$

g) $19 \text{ mA} = \underline{\hspace{2cm}} \text{ A}$

h) $4 \text{ mA} = \underline{\hspace{2cm}} \text{ A}$

i) $27 \text{ mV} = \underline{\hspace{2cm}} \text{ V}$

j) $980 \text{ mV} = \underline{\hspace{2cm}} \text{ V}$

k) $6527 \text{ mV} = \underline{\hspace{2cm}} \text{ V}$


l) $0.2 \text{ V} = \underline{\hspace{2cm}} \text{ mV}$

m) $6 \text{ V} = \underline{\hspace{2cm}} \text{ mV}$

n) $15.5 \text{ V} = \underline{\hspace{2cm}} \text{ mV}$

2) Solve for the unknowns in each circuit.

a)

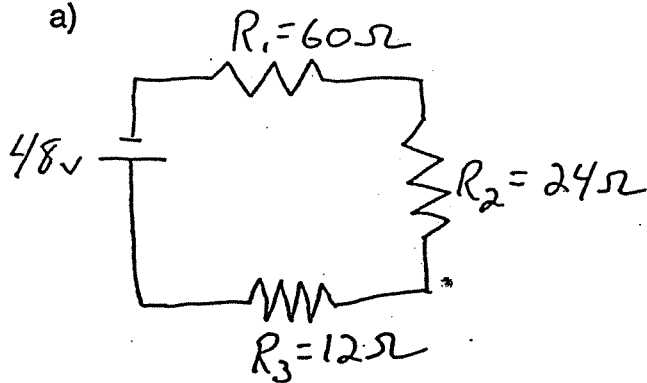

$V_T = \quad R_T = \quad I_T =$

Voltage decrease for R_1 , $V_1 =$


(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$

Total of all Voltage decreases $\underline{\hspace{2cm}}$

b)

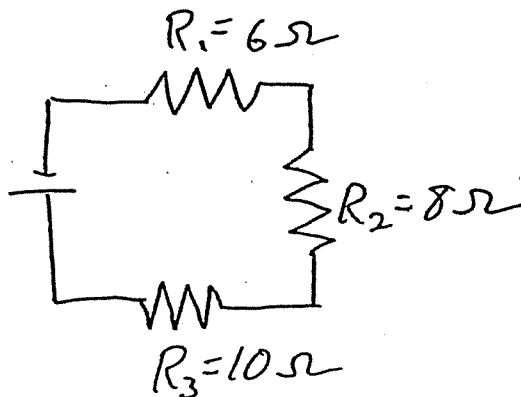

$V_T = \quad R_T = \quad I_T = 0.2 \text{ Amps}$

Voltage decrease for R_1 , $V_1 =$


(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$

Total of all Voltage decreases $\underline{\hspace{2cm}}$

c)

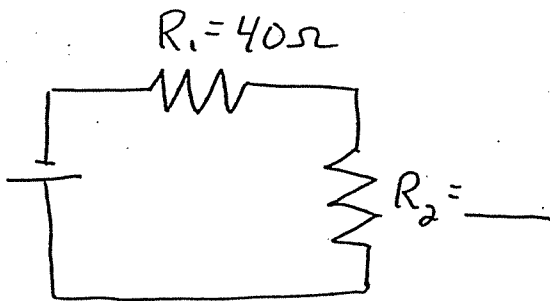

$V_T =$ $R_T =$ $I_T = 3.0 \text{ Amps}$


Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 = 20.0 \text{ v}$

Total of all Voltage decreases ____

d)

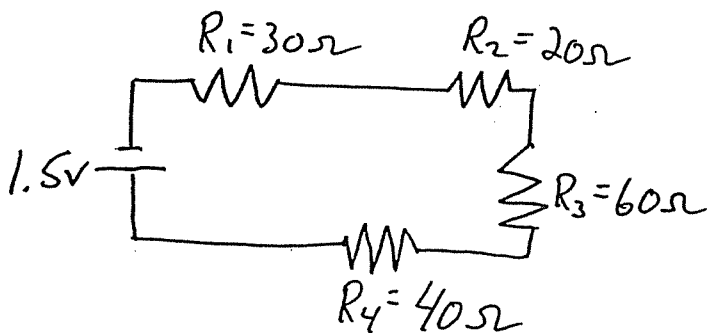

$V_T =$ $R_T =$ $I_T =$

Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)


Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$

Voltage decrease for R_4 , $V_4 =$

Total of all Voltage decreases ____

e)

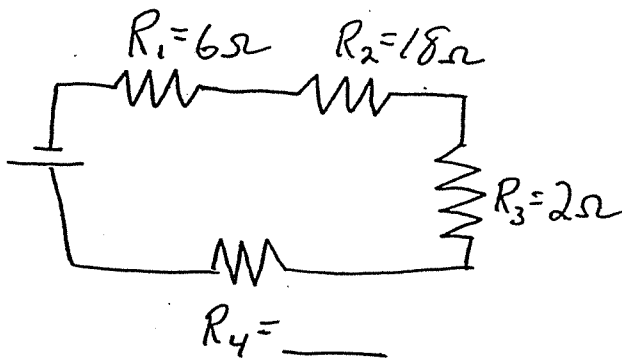

$V_T =$ $R_T =$ $I_T = 2.0 \text{ amps}$

Voltage decrease for R_1 , $V_1 =$

(Remember $V = I \times R$)

Voltage decrease for R_2 , $V_2 =$

Voltage decrease for R_3 , $V_3 =$

Voltage decrease for R_4 , $V_4 =$

Total of all Voltage decreases = 60 v